

Department of Computer Science and Engineering, IIT Delhi
Digital Logic and System Design (COL 215)
I Semester 2022-23
Minor Exam
Maximum Marks: 50
26 Sep 2022, 9:30 to 10:30 AM

1. **[10 Marks]** In two's complement representation:
 - a. What is the representation of integer 8? Use the minimum required number of bits.
 - b. Derive the representation for -8 from the above representation of 8.

01000. Need to use 5 bits. (5 marks)

Representation for -8: (**01000**->10111 + 1 = **11000**). (5 marks)

If using 4 bits for 8 (with representation 1000 for 8, we get 0111+1 = 1000 as representation for -8, which is wrong).

2. **[10 Marks]** How many Boolean functions are there of n variables, in which the function values 0 and 1 are equally likely?

$(2^n)! / ((2^{n-1})!)^2$ [The number of ways of choosing 2^{n-1} 1s in a truth table column of 2^n rows.]

3. **[10 Marks]** The figure below shows an organization of a 5-variable Karnaugh-map suggested by a student in the class. Note that the sequence of cde values form a *Gray code* sequence as we proceed from left to right. After representing the function in this form, is it OK to now apply all our K-map region formation rules? Example of such a rule: start with a cell; every expansion of a region, including an adjacent region (considering “wrap-around” as also adjacent), leads to a term with one less literal. Justify.

No. Any sequence of 4 adjacent cells does not necessarily lead to similar simplifications (e.g., the region highlighted below with $ab=00$ and $cde=010, 110, 111, 101$ doesn't lead to a single-term expression).

Marks will be awarded only if illustrated by a corresponding example (or a formal proof is given).

<div style="display: inline-block; transform: rotate(-45deg);">cde ab</div>		000	001	011	010	110	111	101	100
		00							
	01								
	11								
	10								

4. **[10 Marks]** A 2-bit adder is called a Half-adder because we can put together two half-adders to realise a full-adder. Show how you can use two such half-adders, with minimal additional logic gates, to implement a full-adder.

One half adder generates $S1 = A \text{ XOR } B$, $C1 = AB$

Second half adder generates $S2 = S1 \text{ XOR } C$, $C2 = S1 \text{ AND } C$

FA Sum = $S2$ (4 marks) , Carry = $C1 + C2$ (6 marks)

If the final expression is derived using the truth table without showing the Half adder blocks then marks are deducted.


5. **[10 Marks]** Prove the following theorem of Boolean Algebra starting from the *Postulates* (i.e., no other theorem should be used): $x + xy = x$

$$x + xy = x.1 + xy \quad (2) = x(1+y) \quad (2) = x((y+y')(y+1)) \quad (2) = x(y+y'.1) \quad (2) = x(y+y') \quad (1) = x.1 \quad (1) = x$$

If proved using a theorem then marks are given if theorem proof is shown.

 6. **[10 Marks]** Draw a CMOS circuit (consisting of n- and p-transistors) for implementing the Boolean function: $f = a + bc'$.

- Minimise the number of transistors used in your design.
- Assume that complements of all input variables are available (so, e.g., there is no need to use an inverter to generate c' , since c' is already available as an input).



If AND/NAND/OR/NOR/INV are used instead, then marks are deducted depending on #transistors used.

6 Transistor – 10 marks

7-10 Transistor – 7 marks

>10 Transistor – 5 marks